

2012*Time : 3 hours**Full Marks : 80*

Candidates are required to give their answers in their own words as far as practicable.

The questions are of equal value.

*Answer any **five** questions in which*

Q. No. 1 is compulsory.

1. Choose the correct alternative for the following :

(a) The number of digits in decimal system is :

- (i) 8
- (ii) 10
- (iii) 16
- (iv) 02

2808

(b) The digit B in HEX system is equivalent to _____ in decimal system.

- (i) 13
- (ii) 10

- (iii) 11
(iv) 12
- (c) Which of the following binary numbers is equivalent to decimal 12 ?
(i) 1000 (ii) 1100
(iii) 1010 (iv) 0110
- (d) Which of the following logic families is the fastest ?
(i) RTL (ii) DTL
(iii) ECL (iv) CMOS
- (e) Which of the following gates is the universal gate ?
(i) OR (ii) AND
(iii) NOT (iv) NOR
- (f) Flip-flop basically is a :
(i) Astable multivibrator
(ii) Mono-stable multivibrator
(iii) Bi-stable multivibrator
(iv) None of these
- (g) Which of the following circuits is an example of sequential circuit ?
(i) Adder

- (ii) Multiplexer
 - (iii) Decoder
 - ~~(iv) Flip-flop~~
- (h) How many Flip-flop are required for MOD 6 counter ?
- (i) > 2
 - (ii) 3
 - (iii) 4
 - (iv) 5

2. Minimize the following Boolean function using K-map and implement the logic circuits using NOR gate :

$$f(A, B, C, D) = m \{0, 3, 5, 6, 9, 10, 12, 15\}$$

3. What is multiplexer ? What are the different applications of multiplexer ? Draw 16 : 1 multiplexer using 4 : 1 multiplexer.

4. Draw the logic diagram and construct the excitation table of the following flip-flops :

- (a) Clocked SR flip-flop, JK flip-flop, T flip-flop
- (b) D flip-flop, Master slave JK flip-flop

5. Differentiate between the following :

- (i) Analog Signal and Digital Signal
- (ii) Combinational and Sequential Circuits

(iii) ROM and RAM

(iv) Registers and Counters

6. Explain the working principle with suitable diagram and mention the applications of the following :

(i) Schmitt Trigger

(ii) 555 Timer

7. Realize the following logic operations using NAND gate only :

(i) NOT

(ii) AND

(iii) OR

(iv) XOR

8. Explain different analog to digital converters.

9. Write short notes on any **two** of the following :

(a) Bi-stable Multi-vibrator

(b) Content Addressable Memory

(c) Field Programmable Gate Array

(d) Programmable Logic Array

